

# Bode Plot Analysis of RC Circuits

EE24BTECH11054- Sai Akshitha Suguru  
EE24BTECH11055- Sai Akhila Reddy Turpu

February 18, 2025

## 1 Objective

- Analyze the frequency response of different RC circuits:
  - Single RC circuit
  - Cascaded RC circuit
  - Twice-cascaded RC circuit
- Derive the transfer function  $H(s)$  for each case.
- Apply logarithmic transformation and simplify the expressions.
- Generate magnitude and phase Bode plots to understand system behavior.

## 2 Theory

### 2.1 Transfer Function $H(s)$

The transfer function  $H(s)$  is determined for each RC circuit using circuit analysis techniques. Then, the logarithmic transformation is applied to simplify the expressions for magnitude and phase calculations.

### 2.2 Bode Plot Analysis

Bode plots represent the logarithmic magnitude  $\log |H(s)|$  vs.  $\log \omega$  and the phase response. These plots are useful for understanding the frequency-dependent behavior of the circuits.

## 3 Experimental Setup

### 3.1 Materials Required

- Resistors and capacitors for each circuit configuration. ( $R = 100\Omega$  and  $C = 100\mu\text{F}$ )
- A signal generator to provide input voltage.
- An oscilloscope to measure the output voltage.

### 3.2 Procedure

- Assemble the circuit configurations as per the given schematics.
- Apply an input signal and measure the output at different frequencies.
- Record the voltage gain and phase shift at each frequency.
- Compute the transfer function  $H(s)$  for each configuration.
- Apply logarithmic transformation to obtain magnitude and phase equations.
- Plot the magnitude and phase Bode plots.

## 4 Results and Discussion

### 4.1 Case 1: Single RC Circuit

#### 4.1.1 Circuit Diagram

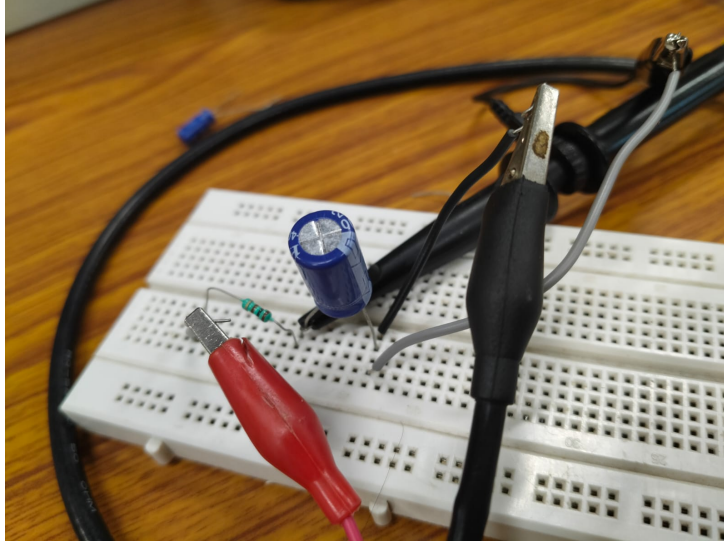


Figure 1: RC Circuit Diagram

#### 4.1.2 Transfer Function

Derived as:

$$H(s) = \frac{1}{1 + sRC} H(j\omega) = \frac{1}{1 + \omega RCj} \quad (1)$$

Applying logarithm:

$$\log |H(j\omega)| = -\frac{1}{2} \log(1 + R^2 C^2 \omega^2) \quad (2)$$

$$\log |H(j\omega)| = -\log(RC) - \frac{1}{2} \log\left(\frac{1}{R^2 C^2} + \omega^2\right) \quad (3)$$

$$20 \log |H(j\omega)| = -20 \log(RC) - 10 \log\left(\frac{1}{R^2 C^2} + \omega^2\right) \quad (4)$$

For nth order circuit, we get

$$\phi = -n \tan^{-1}(RC\omega) \quad (5)$$

We get phase to be :

$$\phi = -\tan^{-1}(RC\omega) \quad (6)$$

## 4.2 Oscilloscope- Practically measured VPP

### 4.2.1 $w = 10$

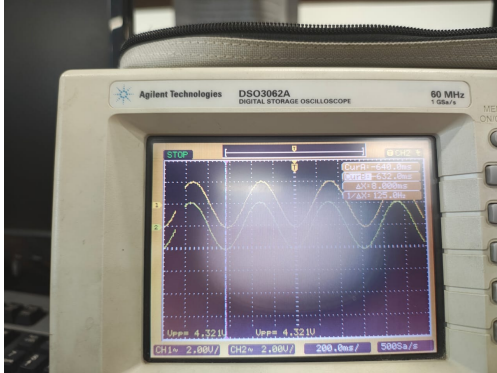


Figure 2: Oscilloscope Reading for  $w = 10$

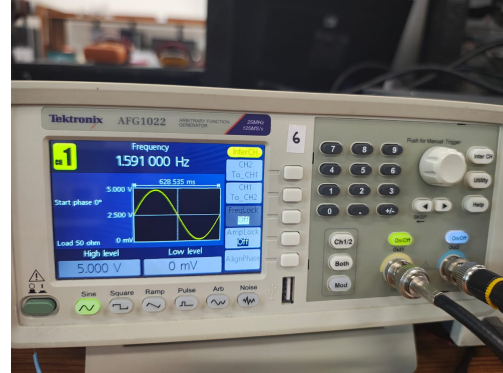


Figure 3: Function Generator Output for  $w = 10$

### 4.2.2 $w = 100$

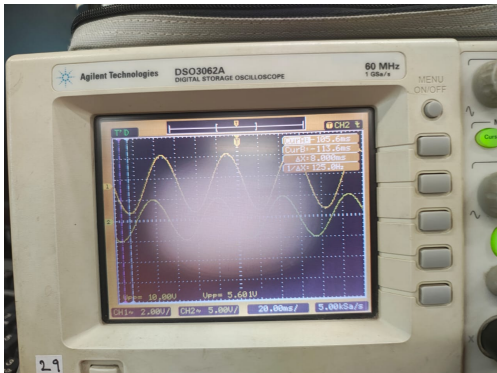


Figure 4: Oscilloscope Reading for  $w = 100$

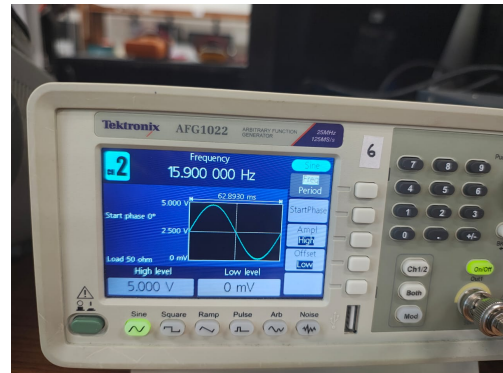


Figure 5: Function Generator Output for  $w = 100$

### 4.2.3 $w = 1000$

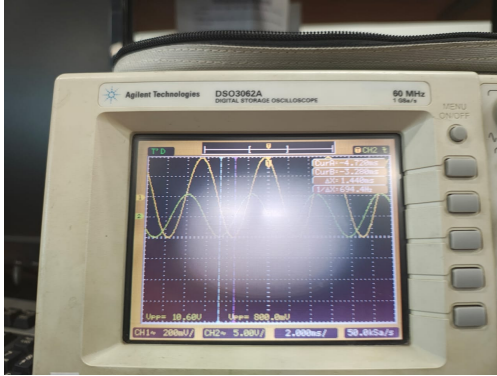


Figure 6: Oscilloscope Reading for  $w = 1000$

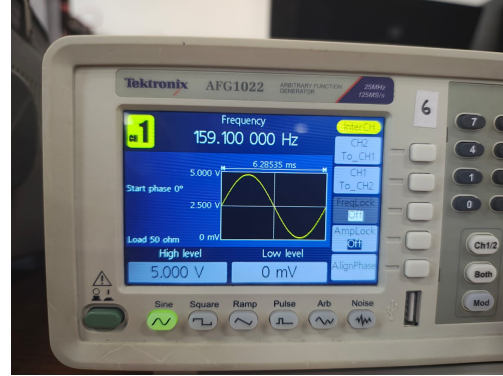


Figure 7: Function Generator Output for  $w = 1000$

## 4.3 Theoretical values

$$\phi = -0.572^\circ,$$

$$\phi = -5.7^\circ,$$

$$\phi = -45^\circ,$$

$$\phi = -84.29^\circ,$$

$$\omega = 10 \text{ rad/s} \quad (7)$$

$$\omega = 10 \text{ rad/s} \quad (8)$$

$$\omega = 100 \text{ rad/s} \quad (9)$$

$$\omega = 1000 \text{ rad/s} \quad (10)$$

## 4.4 Magnitude Bode Plot

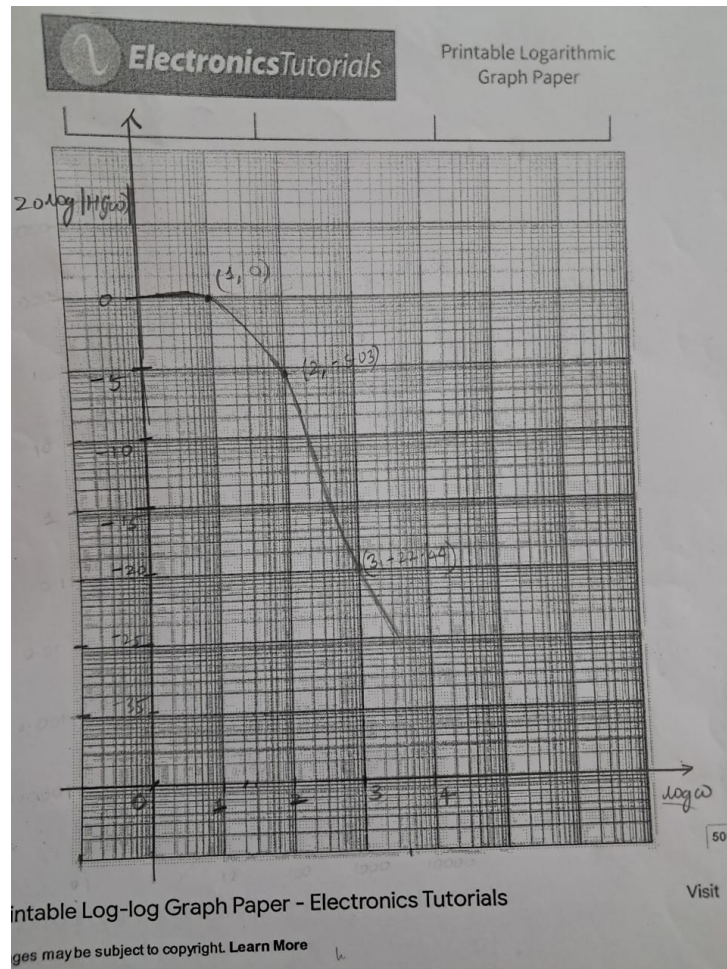


Figure 8: Magnitude Bode Plot for RC Circuit

Magnitude values(measured) are given by:

$$20 \log |H(j\omega)| = 20 \log V_{pp1}/V_{pp2}$$

$$20 \log |H(j\omega)| = 0.00 \text{ dB}, \quad \omega = 10 \text{ rad/s} \quad (11)$$

$$20 \log |H(j\omega)| = -5.0362 \text{ dB}, \quad \omega = 100 \text{ rad/s} \quad (12)$$

$$20 \log |H(j\omega)| = -22.4443 \text{ dB}, \quad \omega = 1000 \text{ rad/s} \quad (13)$$

## 4.5 Phase Bode Plot

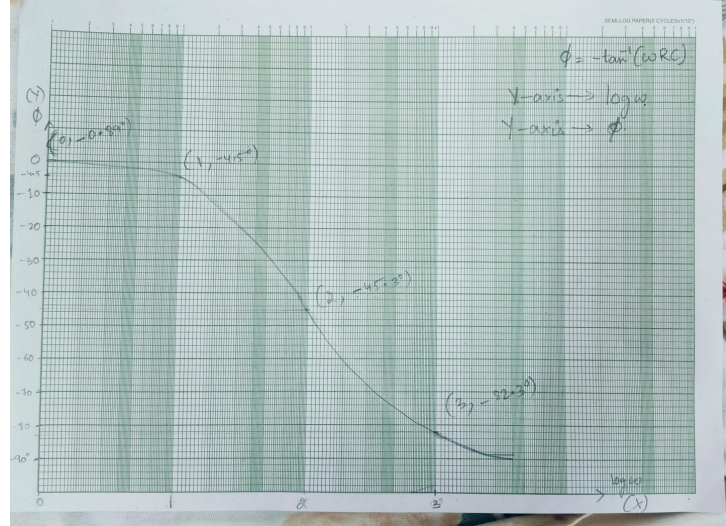


Figure 9: Phase Bode Plot for RC Circuit

Phase difference is given by:

$$\phi = \omega \times \delta t$$

$$\phi = -0.89^\circ, \quad \omega = 1 \text{ rad/s} \quad (14)$$

$$\phi = -4.5^\circ, \quad \omega = 10 \text{ rad/s} \quad (15)$$

$$\phi = -45.3^\circ, \quad \omega = 100 \text{ rad/s} \quad (16)$$

$$\phi = -82.3^\circ, \quad \omega = 1000 \text{ rad/s} \quad (17)$$

## 4.6 Case 2: Cascaded RC Circuit

### 4.6.1 Transfer Function

Derived as:

$$H(j\omega) = \frac{\frac{1}{2RC}}{\frac{1 - \omega^2 R^2 C^2}{2RC} + j\omega} \quad (18)$$

Applying logarithm:

$$\log(|H(j\omega)|) = -\log(2RC) - \frac{1}{2} \left( \log \frac{1 - \omega^2 R^2 C^2}{2RC} \right)^2 + \omega^2 \quad (19)$$



On simplification, we get:

$$20 \log |H(j\omega)| = -40 \log(RC) - 20 \log(\omega^2 + \frac{1}{R^2 C^2}) \quad (20)$$

For nth order circuit, we get

$$\phi = -n \tan^{-1}(RC\omega) \quad (21)$$

We get phase to be :

$$\phi = -2 \tan^{-1}(RC\omega) \quad (22)$$

## 4.7 Oscilloscope- Practically measured VPP

### 4.7.1 $w = 10$

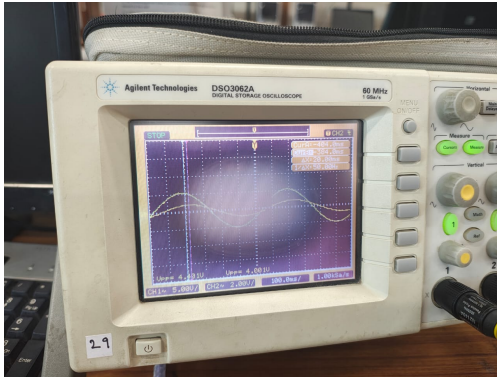


Figure 10: Oscilloscope Reading for  $w = 10$

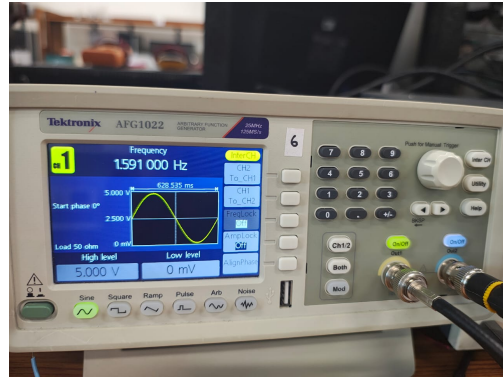


Figure 11: Function Generator Output for  $w = 10$

### 4.7.2 $w = 100$

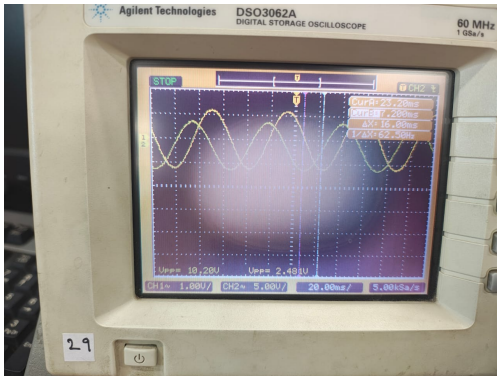


Figure 12: Oscilloscope Reading for  $w = 100$

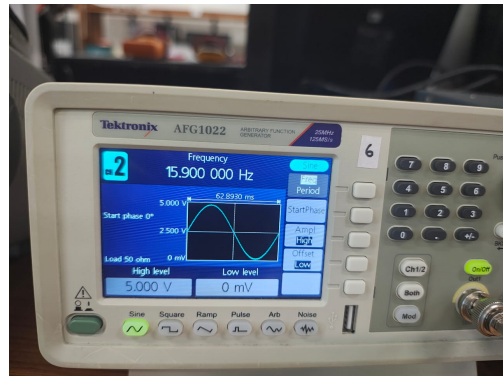


Figure 13: Function Generator Output for  $w = 100$



### 4.7.3 $w = 1000$

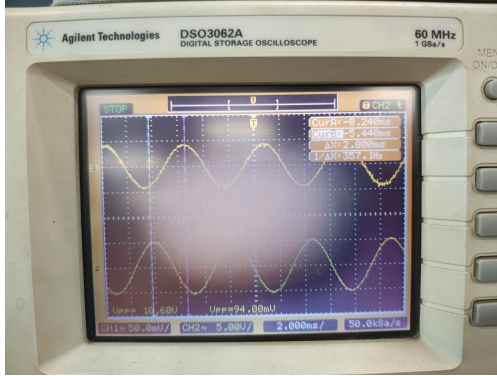


Figure 14: Oscilloscope Reading for  $w = 1000$

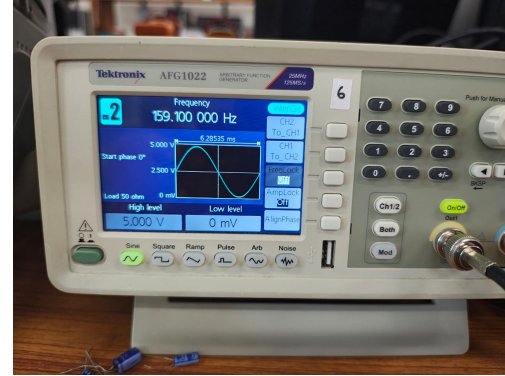


Figure 15: Function Generator Output for  $w = 1000$

## 4.8 Theoretical values

$$\phi = -11.4^\circ,$$

$$\phi = -90^\circ,$$

$$\phi = -168.58^\circ,$$

$$\omega = 10 \text{ rad/s} \quad (23)$$

$$\omega = 100 \text{ rad/s} \quad (24)$$

$$\omega = 1000 \text{ rad/s} \quad (25)$$

## 4.9 Magnitude Bode Plot

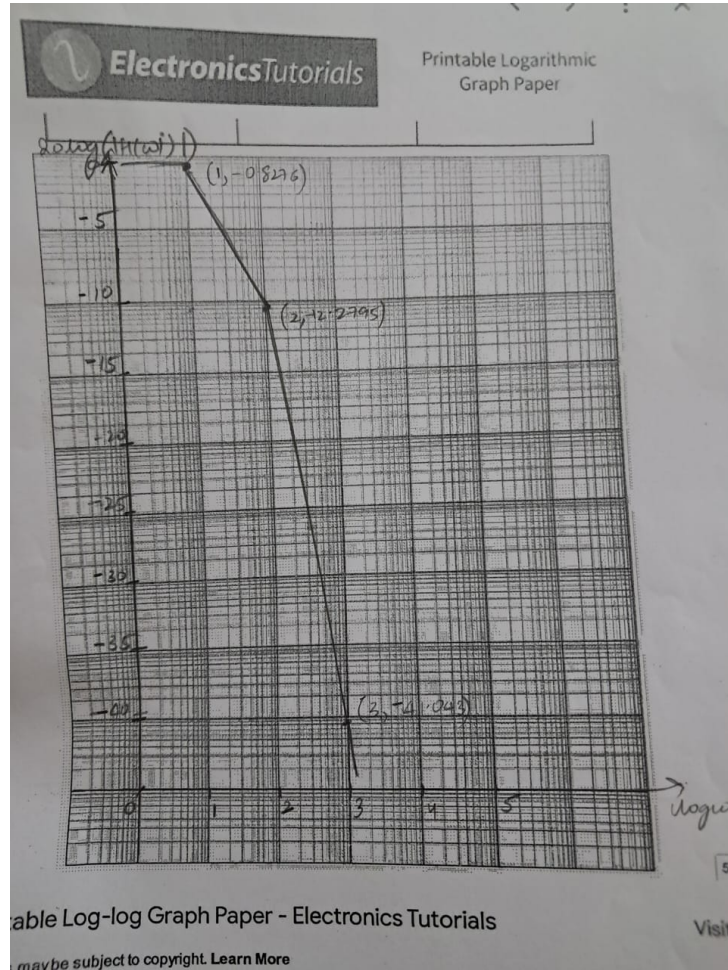


Figure 16: Magnitude Bode Plot for RC Circuit

Magnitude values(measured) are given by:

$$20 \log |H(j\omega)| = 20 \log V_{pp1}/V_{pp2}$$

$$20 \log |H(j\omega)| = -0.8276 \text{ dB}, \quad \omega = 10 \text{ rad/s} \quad (26)$$

$$20 \log |H(j\omega)| = -12.2795 \text{ dB}, \quad \omega = 100 \text{ rad/s} \quad (27)$$

$$20 \log |H(j\omega)| = -41.043 \text{ dB}, \quad \omega = 1000 \text{ rad/s} \quad (28)$$

## 4.10 Phase Bode Plot

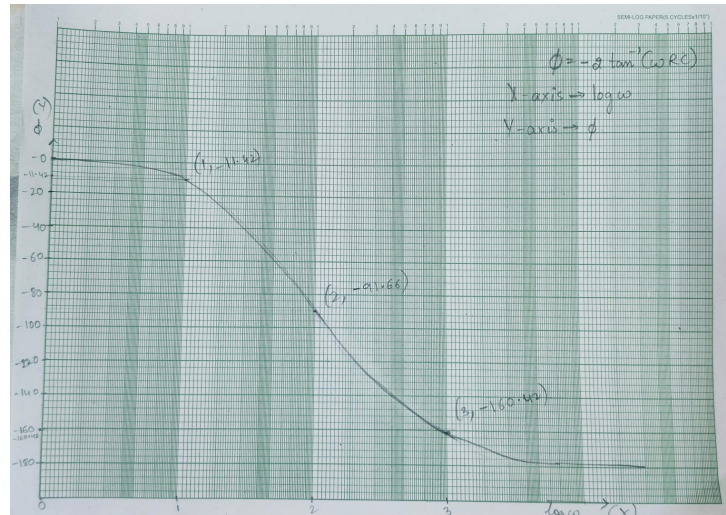


Figure 17: Phase Bode Plot for RC Circuit

Phase difference is given by:

$$\phi = \omega \times \delta t$$

$$\phi = -11.42^\circ, \quad \omega = 10 \text{ rad/s} \quad (29)$$

$$\phi = -91.66^\circ, \quad \omega = 100 \text{ rad/s} \quad (30)$$

$$\phi = -160.42^\circ, \quad \omega = 1000 \text{ rad/s} \quad (31)$$

## 4.11 Case 3: Twice-Cascaded RC Circuit

### 4.11.1 Circuit Diagram

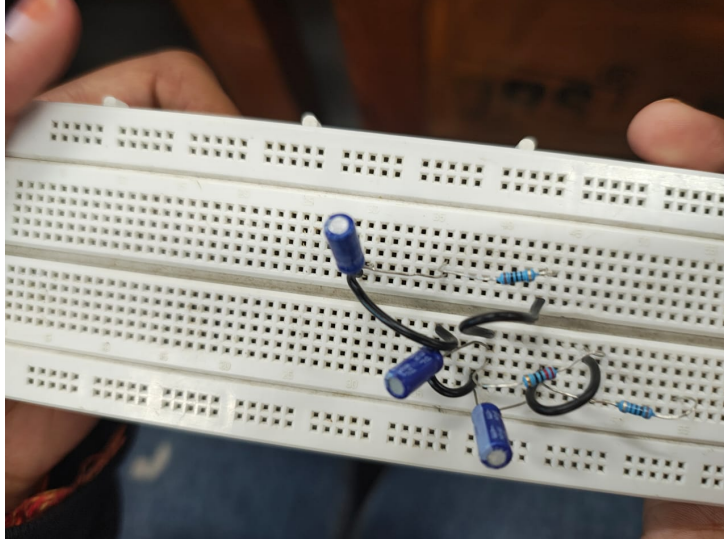


Figure 18: RC Circuit Diagram

### 4.11.2 Transfer Function

Derived as:

$$H(s) = \frac{\frac{1}{3RC + s^2 R^3 C^3}}{\left(\frac{1 + 3s^2 R^2 C^2}{3RC + s^2 R^3 C^3} + s\right)} \quad (32)$$

Since  $s = j\omega$

$$H(j\omega) = \frac{\frac{1}{3RC - \omega^2 R^3 C^3}}{\frac{1 - 3\omega^2 R^2 C^2}{3RC - \omega^2 R^3 C^3} + j\omega} \quad (33)$$

Applying logarithm:

$$\log |H(s)| = -\log(3RC - \omega^2 R^3 C^3) - \frac{1}{2} \log \left( \left( \frac{1 - 3\omega^2 R^2 C^2}{3RC - \omega^2 R^3 C^3} \right)^2 + \omega^2 \right) \quad (34)$$

On simplification, we get:

$$\log |H(s)| = -\frac{3}{2} \left( 2 \log(RC) + \log \left( \omega^2 + \frac{1}{R^2 C^2} \right) \right) \quad (35)$$

$$20 \log |H(s)| = -30 \left( 2 \log(RC) + \log \left( \omega^2 + \frac{1}{R^2 C^2} \right) \right) \quad (36)$$

For nth order circuit, we get

$$\phi = -n \tan^{-1}(RC\omega) \quad (37)$$

We get phase to be :

$$\phi = -3 \tan^{-1}(RC\omega) \quad (38)$$

## 4.12 Oscilloscope - Practically Measured VPP's

### 4.12.1 $w = 10$

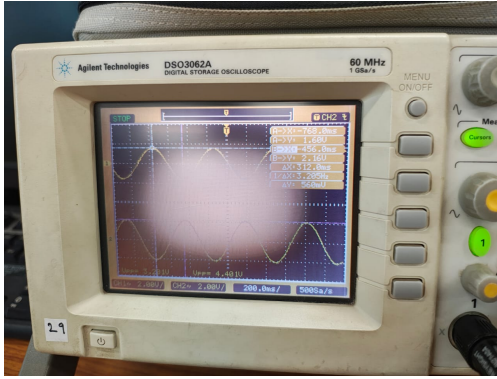


Figure 19: Oscilloscope Reading for  $w = 10$



Figure 20: Function Generator Output for  $w = 10$

### 4.12.2 $w = 100$

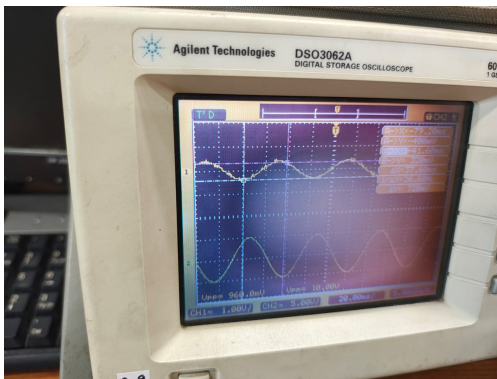


Figure 21: Oscilloscope Reading for  $w = 100$

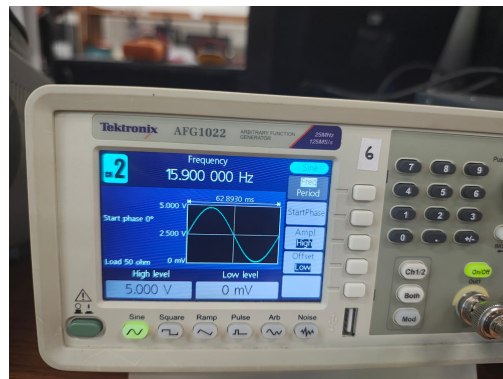


Figure 22: Function Generator Output for  $w = 100$



#### 4.12.3 $w = 1000$

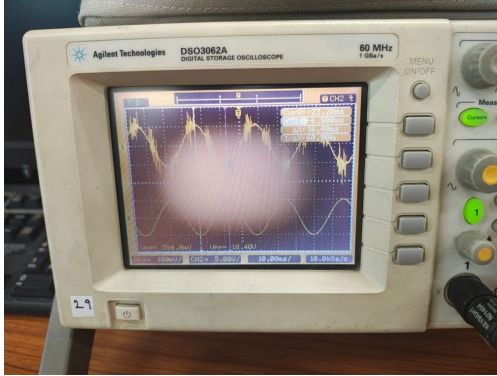


Figure 23: Oscilloscope Reading for  $w = 200$



Figure 24: Function Generator Output for  $w = 200$

### 4.13 Theoretical values

$$\phi = -17.1^\circ,$$

$$\phi = -135^\circ,$$

$$\phi = -252.87^\circ,$$

$$\omega = 10 \text{ rad/s} \quad (39)$$

$$\omega = 100 \text{ rad/s} \quad (40)$$

$$\omega = 1000 \text{ rad/s} \quad (41)$$



## 4.14 Magnitude Bode Plot

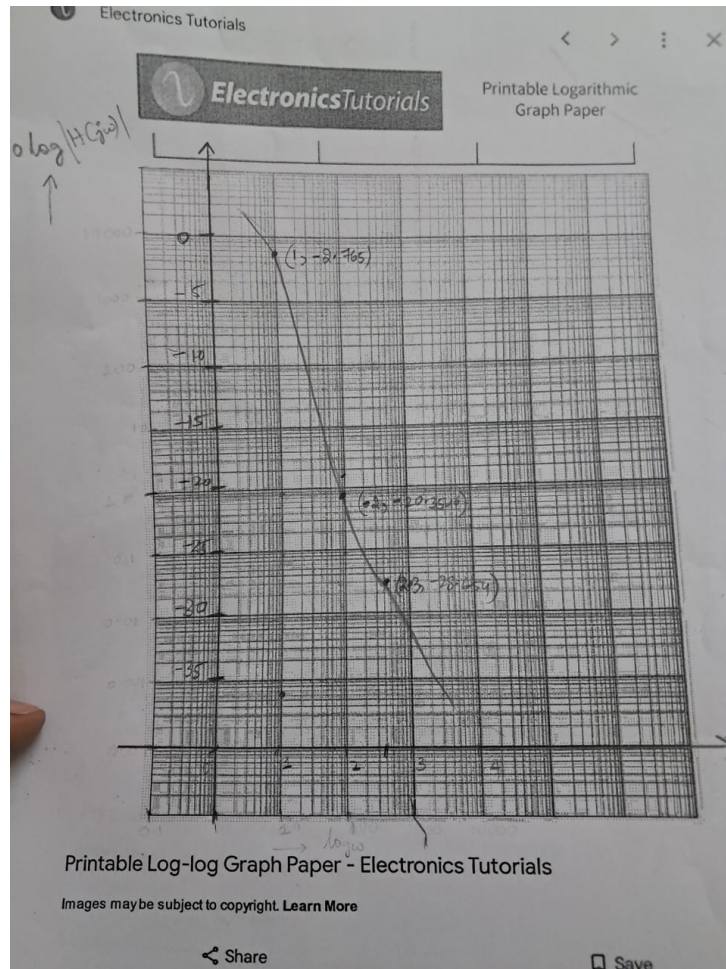


Figure 25: Magnitude Bode Plot for RC Circuit

Magnitude values(measured) are given by:

$$20 \log |H(j\omega)| = 20 \log V_{pp1}/V_{pp2}$$

$$20 \log |H(j\omega)| = -2.765 \text{ dB}, \quad \omega = 10 \text{ rad/s} \quad (42)$$

$$20 \log |H(j\omega)| = -20.3546 \text{ dB}, \quad \omega = 100 \text{ rad/s} \quad (43)$$

$$20 \log |H(j\omega)| = -28.654 \text{ dB}, \quad \omega = 1000 \text{ rad/s} \quad (44)$$

## 4.15 Phase Bode Plot

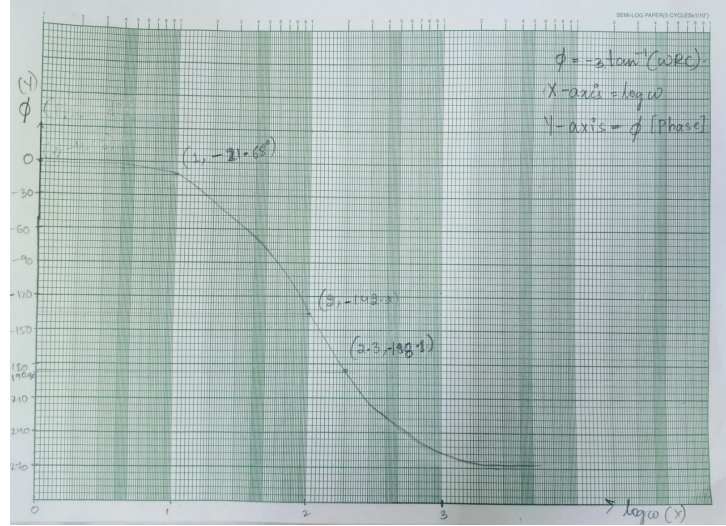


Figure 26: Phase Bode Plot for RC Circuit

Phase difference is given by:

$$\phi = \omega \times \delta t$$

$$\phi = -21.68^\circ, \quad \omega = 10 \text{ rad/s} \quad (45)$$

$$\phi = -142.2^\circ, \quad \omega = 100 \text{ rad/s} \quad (46)$$

$$\phi = -188.1^\circ, \quad \omega = 200 \text{ rad/s} \quad (47)$$

## 5 Conclusion

The results demonstrate how cascading RC circuits affects frequency response. The magnitude plot reveals increasing attenuation with cascading, and phase plots show a shift in phase behavior. These findings are essential in filter design and signal processing applications.